

Relevant Formulas

$Z = R + jX$	(complex impedance)
$X_L = j\omega L$	(reactance of an inductor)
$X_C = \frac{-j}{\omega C}$	(reactance of a capacitor)
$ Z = \sqrt{\Re(Z)^2 + \Im(Z)^2}$	(magnitude of impedance)
$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots$	(series connection)
$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots$	(parallel connection)
$\tilde{V} = V_0 e^{j\omega t}$	(voltage phasor)
$\tilde{I} = I_0 e^{j(\omega t - \phi)} = \frac{\tilde{V}}{Z}$	(current phasor)
$I_0 = \frac{V_0}{ Z }$	(current amplitude)
$\tan \phi = \frac{\Im(Z)}{\Re(Z)}$	(tangent of phase angle)
$\tilde{I}_C = \frac{\tilde{V}_C}{X_C}$	(capacitor current phasor)
$\tilde{I}_L = \frac{\tilde{V}_L}{X_L}$	(inductor current phasor)
$\phi = 0$	(resonance condition)
$P_{av} = \frac{I_0 V_0}{2} \cos \phi = I_{rms} V_{rms} \cos \phi$	(average power)
$P_{av,R} = I_{rms}^2 R$	(average power dissipated in resistor)

In simple (all parallel or all series) AC RLC Circuits, a helpful mnemonic is:

ELI the *ICE* man

In inductors, current lags voltage by $\pi/2$ and in capacitors, current leads voltage by $\pi/2$, and in resistors, in phase with the voltage

Therefore:

$$\tilde{I}_L = I_{0,L} e^{j(\omega t - \frac{\pi}{2})}$$


$$\tilde{I}_C = I_{0,C} e^{j(\omega t + \frac{\pi}{2})}$$

$$\tilde{I}_R = I_{0,R} e^{j(\omega t)}$$

Problem 1. RCL circuit

In the given circuit, calculate the current in each circuit element given that

$$V = V_0 \sin(\omega t)$$

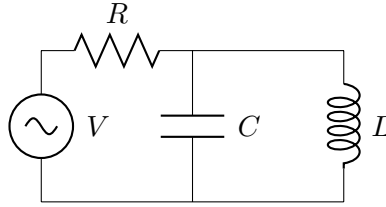

- Find the complex impedance Z .
- Find the current phasors in the 3 circuit elements.

Solution**Part (a)**

We know that that

$$Z = R + jX$$

The impedances of the circuit elements are:

$$X_L = j\omega L$$

and

$$X_C = \frac{-j}{\omega C}$$

We first find the complex impedance of the parallel LC combination

$$1/Z_{LC} = 1/X_L + 1/X_C = \frac{-j}{\omega L} + j\omega C$$

$$1/Z_{LC} = j \frac{\omega^2 LC - 1}{\omega L}$$

$$Z_{XL} = j \left(\frac{\omega L}{1 - \omega^2 LC} \right)$$

We can then find the complex impedance of the entire system:

$$Z = R + Z_{XL} = R + j \left(\frac{\omega L}{1 - \omega^2 LC} \right)$$

$$\boxed{Z = R + j \left(\frac{\omega L}{1 - \omega^2 LC} \right)}$$

Knowing that:

$$|Z| = \sqrt{\Re(Z)^2 + \Im(Z)^2}$$

We can calculate the impedance of the circuit:

$$|Z| = \sqrt{R^2 + \frac{\omega^2 L^2}{(1 - \omega^2 LC)^2}}$$

Knowing that:

$$\tan(\phi) = \frac{\Im(Z)}{\Re(Z)}$$

We can calculate the tangent of the phase angle ϕ :

$$\tan(\phi) = \frac{\omega L}{R(1 - \omega^2 LC)}$$

Part (b)

We can represent the current in the circuit as a whole and the voltage of the source as phasors:

$$\tilde{V} = V_0 e^{j\omega t}$$

$$\tilde{I} = I_0 e^{j(\omega t - \phi)}$$

Where

$$I_0 = \frac{V_0}{|Z|}$$

Since R is in series with the LC combination, we know that

$$\tilde{I}_R = \tilde{I}_C + \tilde{I}_L = \tilde{I} = \frac{V_0}{|Z|} e^{j(\omega t - \phi)}$$

$$\boxed{\tilde{I}_R = \frac{V_0}{|Z|} e^{j(\omega t - \phi)}}$$

Since C and L are in parallel, they have the same voltage. Since they are in series with R

$$\tilde{V}_C = \tilde{V}_L = \tilde{V} - \tilde{V}_R$$

$$\tilde{V}_C = V_0 e^{j\omega t} - \frac{RV_0}{|Z|} e^{j(\omega t - \phi)}$$

$$\tilde{V}_C = V_0 e^{j\omega t} \left(1 - \frac{R}{|Z|} e^{-j\phi}\right)$$

We know that:

$$\tilde{I}_C = \frac{\tilde{V}_C}{X_C}$$

Therefore we can deduce that:

$$\tilde{I}_C = V_0 e^{j\omega t} \left(1 - \frac{R}{|Z|} e^{-j\phi}\right) (j\omega C); \quad j = e^{j\frac{\pi}{2}}$$

$$\boxed{\tilde{I}_C = V_0 \omega C e^{j(\omega t + \frac{\pi}{2})} \left(1 - \frac{R}{|Z|} e^{-j\phi}\right)}$$

We know that:

$$\tilde{I}_L = \frac{\tilde{V}_C}{X_L}$$

Therefore we can deduce that:

$$\tilde{I}_L = V_0 e^{j\omega t} \left(1 - \frac{R}{|Z|} e^{-j\phi}\right) \left(\frac{-j}{\omega L}\right); \quad -j = e^{j\frac{-\pi}{2}}$$

$$\boxed{\tilde{I}_L = \frac{V_0}{\omega L} e^{j(\omega t - \frac{\pi}{2})} \left(1 - \frac{R}{|Z|} e^{-j\phi}\right)}$$